

361-1-4201

Computer Architecture

Intro to Microarchitecture: Single-Cycle, Multi-Cycle

Dr. Guy Tel-Zur

Based on slides by Prof. Onur Mutlu

Spring 2015

and

H&H Chapter 7

Agenda for Today & Next Few Lectures

- Start Microarchitecture
- Single-cycle Microarchitectures
- Multi-cycle Microarchitectures
- Microprogrammed Microarchitectures
- Pipelining
- Issues in Pipelining: Control & Data Dependence Handling, State Maintenance and Recovery, ...

Lectures 4-5

Lecture 6

Lect 7

Recap of the Last Lectures

- Computer Architecture Today and Basics – Lecture #1
- Fundamental Concepts – Lecture #1
 - Computer Arch = ISA (the definition) + uArch (the implementation)
- ISA basics and tradeoffs – Lecture #2
 - Instruction length
 - Uniform vs. non-uniform decode
 - Number of registers
 - Addressing modes
 - Aligned vs. unaligned access
 - RISC vs. CISC properties
- RISC-V ISA – Lecture #3
 - RISC-V ISA Overview
- Datapath & Control, and an introduction to Pipeline – Lecture #4

חומרים למחשבה

- As you learn the RISC-V ISA, think about what **tradeoffs** the designers have made
 - in terms of the ISA properties we talked about
- And, think about the **pros and cons** of design choices
 - In comparison to ARM, Alpha
 - In comparison to x86, VAX
- And, think about the **potential mistakes**
 - Branch delay slot? (טרם למדנו – stall in the pipeline)
 - Load delay slot? (להבטיח שההוראה הבאה תתבצע ללא עיכוב)
 - No FP, no multiply, MIPS (initial)

עוד חומר למחשבה Food for Thought for You

- How would you design a new ISA?
- Where would you place it?
- What design choices would you make in terms of ISA properties?
- What would be the first question you ask in this process?
 - “What is my **design point**?”
 - The 1st question to ask what is the Design Point / Use Case
מה השאלה הראשונה שתמצו לשאול את המזמין

Review: Other Example ISA-level Tradeoffs

- Condition codes vs. not – יילמד בהמשך
- VLIW vs. single instruction – אם נספיק יילמד בהמשך
- SIMD (single instruction multiple data) vs. SISD – הטקסונומיה של פלין
- Precise vs. imprecise exceptions – יילמד בהמשך
- Virtual memory vs. not
- Unaligned access vs. not
- Hardware interlocks vs. software-guaranteed interlocking
- Software vs. hardware managed page fault handling - לא יילמד
- Cache coherence (hardware vs. software) – לא יילמד

... **היכן למקם את המעמסה Think Programmer vs. (Micro)architect**

Review: A Note on RISC vs. CISC

■ RISC

- Simple instructions
- Fixed length
- Uniform decode
- Few addressing modes

■ CISC

- Complex instructions
- Variable length
- Non-uniform decode
- Many addressing modes

Now That We Have an ISA


- How do we implement it?
- i.e., how do we design a system that obeys the hardware/software interface?
- Aside: “System” can be solely hardware or a combination of hardware and software
 - Remember “Translation of ISAs”
 - A virtual ISA can be converted by “software” into an implementation ISA
- We will assume “hardware” for most lectures

Implementing the ISA: Microarchitecture Basics


How Does a Machine Process Instructions?

- What does processing an instruction mean?
- Remember the von Neumann model

 AS = Architectural (programmer visible) state before an instruction is processed



Process instruction

 


AS' = Architectural (programmer visible) state after an instruction is processed

- Processing an instruction: Transforming AS to AS' according to the ISA specification of the instruction

Remember: Programmer Visible (Architectural) State


הגדרת AS

 

Memory

array of storage locations

indexed by an address

 

Registers

- given special names in the ISA (as opposed to addresses)
- general vs. special purpose

Program Counter

memory address

of the current instruction

Instructions (and programs) specify how to transform
the values of programmer visible state

הערה לעצמי: הדגמת דבאגר

/home/telzur/science/Teaching/CPU/lectures/05/code/
ddd_demo.c

The “Process instruction” Step

- ISA specifies abstractly what AS' should be, given an instruction and AS

- It defines an abstract **finite state machine** where

Finite State Machine

- **State** = programmer-visible state
- Next-state logic = instruction execution specification

- From ISA point of view, there are no “intermediate states” between AS and AS' during instruction execution

- One state transition per instruction

AS = Architecture State

MS=Microarchitecture State

- Microarchitecture implements how AS is transformed to AS'

- There are many choices in implementation
- We can have programmer-invisible state to optimize the speed of instruction execution: multiple state transitions per instruction

- Choice 1: AS → AS' (transform AS to AS' in a single clock cycle)


- Choice 2: AS → AS+MS1 → AS+MS2 → AS+MS3 → AS' (take multiple clock cycles to transform AS to AS')

A Very Basic Instruction Processing Engine


- Each instruction takes a single clock cycle to execute
- Only **combinational logic** is used to implement instruction execution
 - *No intermediate, programmer-invisible state updates*



 AS = Architectural (programmer visible) state
at the beginning of a clock cycle




Process instruction in one clock cycle

 

AS' = Architectural (programmer visible) state
at the end of a clock cycle

A Very Basic Instruction Processing Engine

- Single-cycle machine

 

נשאל 2 שאלות,
מישהו רוצה לענות?

- What is the *clock cycle time* determined by?
- What is the *critical path* of the combinational logic determined by?

Single-cycle vs. Multi-cycle Machines

- **Single-cycle machines**
 - Each instruction takes a single clock cycle
 - All state updates made at the end of an instruction's execution
 - Big disadvantage: The slowest instruction determines cycle time 📧 long clock cycle time
- **Multi-cycle machines**
 - Instruction processing broken into multiple cycles (or stages)
 - State updates can be made during an instruction's execution
 - Architectural state(*) updates made only at the end of an instruction's execution
 - Advantage over single-cycle: The slowest "stage" determines cycle time
- Both single-cycle and multi-cycle machines literally follow the von Neumann model at the microarchitecture level

Instruction Processing “Cycle”

- Instructions are processed under the direction of a “control unit” step by step.
- Instruction cycle: Sequence of steps to process an instruction
- Fundamentally, there are six phases (steps):

- Fetch

- Decode

- Evaluate Address

- Fetch Operands

- Execute

- Store Result

→ Not all instructions
require all six stages

- IF - Fetch

- ID - Decode

- EX - Execute/Evaluate Address

- MEM - Fetch Operands

- WB - Store Result

We will later change to 5 stages

יש להבחין בין משך של הוראה, לבין שלב של הוראה, ולבין זמן מחזור של שעון!

Instruction Processing “Cycle” vs. Machine Clock Cycle

- Single-cycle machine:
 - All six phases of the instruction processing cycle take a *single machine clock cycle* to complete
- Multi-cycle machine:
 - All six phases of the instruction processing cycle can take *multiple machine clock cycles* to complete
 - In fact, *each phase can take multiple clock cycles to complete*

למשל יתכן שביצוע FETCH יקח 5 מחזורי שעון...

□ האינטראקציה בין המעבד לזכרון במחשב מסוג single cycle היא בעייתית...

Instruction Processing Viewed Another Way

Data vs. Control
separation

- Instructions transform **Data** (AS) to **Data'** (AS')
- This transformation is done by **functional units**
 - Units that “operate” on data
- These units need to be told what to do to the data
- An instruction processing engine consists of two components
 - **Datapath**: Consists of hardware elements that deal with and transform data signals
 - functional units that operate on data
 - hardware structures (e.g. wires and muxes) that enable the flow of data into the functional units and registers
 - storage units that store data (e.g., registers)
 - **Control logic**: Consists of hardware elements that determine control signals, i.e., signals that specify what the datapath elements should do to the data

Single-cycle vs. Multi-cycle: Control & Data

- **Single-cycle machine:**

- Control signals are generated in the same clock cycle as the one during which data signals are operated on
- Everything related to an instruction happens in one clock cycle (serialized processing)

- **Multi-cycle machine:**

- Control signals needed in the next cycle can be generated in the current cycle
- Latency of control processing can be overlapped with latency of datapath operation (more parallelism)

- We will see the difference clearly in *microprogrammed multi-cycle microarchitectures*

Many Ways of Datapath and Control Design

- There are many ways of designing the data path and control logic
- Single-cycle, multi-cycle, pipelined datapath and control
- Single-bus vs. multi-bus datapaths
- Hardwired/combinational vs. microcoded/microprogrammed control(*)
 - Control signals generated by combinational logic versus
 - Control signals stored in a memory structure
- Control signals and structure depend on the datapath design

Performance Analysis

$$\text{CPI} = 1/\text{IPC}$$

- Execution time of an instruction
 - $\{\text{CPI}\} \times \{\text{clock cycle time}\}$
- Execution time of a program
 - Sum over all instructions $[\{\text{CPI}\} \times \{\text{clock cycle time}\}]$
 - $\{\# \text{ of instructions}\} \times \{\text{Average CPI}\} \times \{\text{clock cycle time}\}$
- Single cycle microarchitecture performance
 - $\text{CPI} = 1$
 - Clock cycle time = long
- Multi-cycle microarchitecture performance
 - $\text{CPI} = \text{different for each instruction}$
 - Average CPI 📧 hopefully small
 - Clock cycle time = short

In single cycle we have
one degree of freedom
to optimize


In multi-cycle we have
two degrees of freedom
to optimize independently
ניתן "לשחק" עם 2 גדלים:
CPI ו- clock cycle time

A Single-Cycle Microarchitecture


A Closer Look

Remember...

- Single-cycle machine

 




- Single-cycle machine

 

Let's Start with the State Elements

■ Data and control inputs

   נתחיל עם כל מה שהוא
programmer visible state



For Now, We Will Assume




- “Magic” memory and register file
- Combinational read
 - output of the read data port is a combinational function of the register file contents and the corresponding read select port

- Synchronous write

- the selected register is updated on the **positive** edge clock transition when write enable is asserted

 - Cannot affect read output in between clock edges



- Single-cycle, synchronous memory – זוהי הנחה לשם הפשטות

- Contrast this with memory that tells when the data is ready
- i.e., Ready bit: indicating the read or write is done

 


FIGURE 4.3 Combinational logic, state elements, and the clock are closely related. In a synchronous digital system, the clock determines when elements with state will write values into internal storage. Any inputs to a state element must reach a stable value (that is, have reached a value from which they will not change until after the clock edge) before the active clock edge causes the state to be updated. All state elements in this chapter, including memory, are assumed to be **positive edge-triggered**; that is, they change on the rising clock edge.

Instruction Processing

- 5 generic steps (P&H book) –

אמנם דיברנו על 6 שלבים אך כאן נעשה מיזוג ושינוי קל לעומת מה שנכתב לפני מספר שקפים


Instruction fetch (IF) ☐

Instruction decode and register operand fetch (ID/RF = Register Fetch) ☐

Execute/Evaluate memory address (EX/AG = Address Generate) ☐


Memory operand fetch (MEM) ☐

Store/writeback result (WB) ☐

 

What Is To Come: The Full MIPS(*) Datapath

 (* RISC-V is quite similar except the wires numbering)




Single-Cycle Datapath for *Arithmetic and Logical Instructions*

R-Type ALU Instructions (MIPS)

- Assembly (e.g., register-register signed addition)

ADD rd_{reg} rs_{reg} rt_{reg}

- Machine encoding

 

- Semantics


if MEM[PC] == ADD rd rs rt

אם מה שנמצא בזיכרון בכתובת
PC שווה לתוכן שבאגף ימין אז...

$GPR[rd] \leftarrow GPR[rs] + GPR[rt]$

$PC \leftarrow PC + 4$

להלן המימוש ALU Datapath

 

if MEM[PC] == ADD rd rs rt

GPR[rd] ← GPR[rs] + GPR[rt]

PC ← PC + 4 (assuming no compressed instructions support)


IF ID EX MEM WB




Combinational
state update logic

להלן המימוש R-Type ALU

אנימציה

 

 
$GPR[rd] \leftarrow GPR[rs] + GPR[rt]$
 $PC \leftarrow PC + 4$



Combinational
state update logic

The General-Purpose Register file (GPR file). This unit is required for the decode phase (and for the Write Back phase)

 It includes the
32 registers the
programmer can
access (\$0 - \$31)



Let's see how it is used:

The General-Purpose Register file (GPR).

There are 3 ports in this box

If we want to read from \$7 via port 1


we set Read register1 to 7 = 00111

we then gets the contents of \$7 at the

Read data1 output

we mark it as: GPR[7]

It could be 103 for example

 

The General-Purpose Register file (GPR).

So if we have the instruction:

add \$12, \$7, \$2

we connect the Rs field Read reg1

Rs Rt

and get GPR[Rs] at the Read data1 output

In our case we assumed GPR[7]=103


In our case we also assume

assumed that GPR[2]=62

we connect the Rt field Read register2

and get GPR[Rt] at the

Read data2 output

 

R


opcode	rs	rt	rd	shamt	funct
31	26 25	21 20	16 15	11 10	6 5 0

So this is the real picture:

add \$12, \$7, \$2

So we did $GPR[R_d] = GPR[R_s] + GPR[R_t]$

i.e., $GPR[12]=GPR[7]+GPR[2]$

 

So what's next? We want to add the 103 & 62 $103 + 62 = 165$


Now we want to write this to Rd

I-Type ALU Instructions

- Assembly (e.g., register-immediate signed additions)

ADDI rt_{reg} rs_{reg} $immediate_{16}$

- Machine encoding

 

I-type

- Semantics


if $MEM[PC] == \text{ADDI } rt \ rs \ immediate$

$GPR[rt] \leftarrow GPR[rs] + \text{sign-extend}(immediate)$

$PC \leftarrow PC + 4$

Datapath for R and I-Type ALU Insts.

אנימציה

 

המוקס נועד גם לתמוך בהוראת R וגם
לאפשר לרגיסטר 2 להיות היעד לכתיבה

בהוראת I.

if MEM[PC] == ADDI rt rs immediate

GPR[rt] ← GPR[rs] + sign-extend (immediate)


PC ← PC + 4

IF ID EX MEM WB

Combinational
state update logic

Datapath for R and I-Type ALU Insts.

אנימציה

 

$GPR[rt] \oplus GPR[rs] + \text{sign-extend}(\text{immediate})$

$PC \oplus PC + 4$



Combinational
state update logic

Single-Cycle Datapath for *Data Movement Instructions*

Load Instructions


- Assembly (e.g., load 4-byte word)

$\text{LW } r_{\text{reg}} \text{ offset}_{16} (\text{base}_{\text{reg}})$

כמו rs

Load
הוא ממשפחת ה-I-type

- Machine encoding

 

I-type

- Semantics


if $\text{MEM}[\text{PC}] = \text{LW } r_{\text{reg}} \text{ offset}_{16} (\text{base})$

$\text{EA} = \text{sign-extend}(\text{offset}) + \text{GPR}[\text{base}]$

$\text{GPR}[\text{rt}] \leftarrow \text{MEM}[\text{translate}(\text{EA})]$

$\text{PC} \leftarrow \text{PC} + 4$

LW Datapath

 

if $MEM[PC] == LW \text{ rt offset}_{16} \text{ (base)}$

$EA = \text{sign-extend}(\text{offset}) + GPR[\text{base}]$

$GPR[\text{rt}] \leftarrow MEM[\text{translate}(EA)]$


$PC \leftarrow PC + 4$

IF ID EX MEM WB

Combinational
state update logic

LW Datapath

אנימציה

 

$$EA = GPR[rs] + \text{sign-extend}(\text{offset})$$

$$GPR[rt] \oplus MEM[EA]$$

$$PC \oplus PC + 4$$



Combinational
state update logic


Store Instructions

- Assembly (e.g., store 4-byte word)

$SW\ rt_{reg}\ offset_{16}\ (base_{reg})$

rs imm

- Machine encoding

 

I-type

- Semantics


if $MEM[PC] == SW\ rt\ offset_{16}\ (base)$

$EA = \text{sign-extend}(\text{offset}) + GPR[\text{base}]$

$MEM[\text{translate}(EA)] \oplus GPR[\text{rt}]$

$PC \oplus PC + 4$

SW Datapath

 

if $MEM[PC] == SW \text{ rt offset}_{16}(\text{base})$

$EA = \text{sign-extend}(\text{offset}) + GPR[\text{base}]$

$MEM[\text{translate}(EA)] \oplus GPR[\text{rt}]$

$PC \oplus PC + 4$


IF ID EX MEM WB

Combinational
state update logic


אנימציה



Load-Store Datapath

 

 Datapath for Non-Control-Flow Instructions



שם המולטיפלקסר → MemtoReg
 שם אות הבקרה → isLoad



חזרה והסבר נוסף על ה- datapath עבור ההוראות שנלמדו עד-כה
ניתנת מחדש ב-7 השקפים הבאים הלקוחים מ-

CSE378 University of Washington

[/courses.cs.washington.edu/courses/cse378/10sp/lec.html](https://courses.cs.washington.edu/courses/cse378/10sp/lec.html)

-במידה ולא נתעכב עליהם כאן והמעבר על השקפים יעשה בלימוד
עצמי בבית-

Encoding R-type instructions

- Last lecture, we saw encodings of MIPS instructions as 32-bit values.
- Register-to-register arithmetic instructions use the **R-type** format.
 - **op** is the instruction opcode, and **func** specifies a particular arithmetic operation (see textbook).
 - **rs**, **rt** and **rd** are source and destination registers.

op	rs	rt	rd	shamt	func
6 bits	5 bits	5 bits	5 bits	5 bits	6 bits


- An example instruction and its encoding:

add \$s4, \$t1, \$t2

000000	01001	01010	10100	00000	1000000
--------	-------	-------	-------	-------	---------

Registers and ALUs

 
- R-type instructions must access registers and an ALU.
- Our **register file** stores thirty-two 32-bit values.
 - Each register specifier is 5 bits long.
 - You can read from two registers at a time.
 - **RegWrite** is 1 if a register should be written.



- Here's a simple **ALU** with five operations, selected by a 3-bit control signal **ALUOp**.


להמחשה בלבד

ALUOp	Function
000	and
001	or
010	add
110	subtract
111	slt

 

Executing an R-type instruction

1. Read an instruction from the instruction memory.
2. The source registers, specified by instruction fields **rs** and **rt**, should be read from the register file.
3. The ALU performs the desired operation.
4. Its result is stored in the destination register, which is specified by field **rd** of the instruction word.

 

Encoding I-type instructions

- The lw, sw and beq instructions all use the **I-type** encoding.
 - **rt** is the *destination* for lw, but a *source* for beq and sw.
 - **address** is a 16-bit signed constant.

op	rs	rt	address
6 bits	5 bits	5 bits	16 bits

\$SP הוא רגיסטר מספר 29

t0 הוא רגיסטר מספר 8

- Two example instructions:

lw \$t0, -4(\$sp)


100011	11101	01000	1111 1111 1111 1100
--------	-------	-------	---------------------

sw \$a0, 16(\$sp)

101011	11101	00100	0000 0000 0001 0000
--------	-------	-------	---------------------


Accessing data memory

- For an instruction like `lw $t0, -4($sp)`, the base register `$sp` is added to the *sign-extended* constant to get a data memory address.
- This means the ALU must accept *either* a register operand for arithmetic instructions, *or* a sign-extended immediate operand for `lw` and `sw`.
- We'll add a multiplexer, controlled by `ALUSrc`, to select either a register operand (0) or a constant operand (1).

 

MemToReg

 - The register file's "Write data" input has a similar problem. It must be able to store *either* the ALU output of R-type instructions, *or* the data memory output for lw.
- We add a mux, controlled by **MemToReg**, to select between saving the ALU result (0) or the data memory output (1) to the registers.




RegDst

- A final annoyance is the destination register of lw is in *rt* instead of *rd*.

op	rs	rt	address
----	----	----	---------

lw \$rt, address(\$rs)

 - We'll add one more mux, controlled by **RegDst**, to select the destination register from either instruction field *rt* (0) or field *rd* (1).



עד כאן תוספת שקפים מתוך CSE378


Single-Cycle Datapath for *Control Flow Instructions*

Unconditional Jump Instructions (MIPS)

- Assembly

J immediate₂₆

- Machine encoding

 

J-type

- Semantics

if MEM[PC]==J immediate₂₆

target = { PC[31:28], immediate₂₆, 2'b00 }

PC  target

Guy> This is the addressing mode convention:
[concatenate the PC+imm+2'b00]

4 ביטים עליונים == הספרה השמאלית של ה-PC בבסיס 16

לת * תזכורת מפת זיכרון ה- MIPS (*)

MEMORY ALLOCATION


\$sp → 7fff fffc_{hex}

\$gp → 1000 8000_{hex}

1000 0000_{hex}

pc → 0040 0000_{hex}

0_{hex}

 

$$16^7 = 2^{28} = 256\text{M}$$

Text size = 252M

400000hex=4M

* מפת הזיכרון עבור
RISC-V הוצגה
בשיעור 3 (פרק 6
H&H, וגם היא
לימודית ולא מחייבת)


Unconditional Jump Datapath (MIPS)

אנימציה

שימו לב:

J וגם JAL הן הוראות ממשפחת I

לעומת זאת JR היא ממשפחת R

 

**Based on original figure from [P&H CO&D, COPYRIGHT 2004 Elsevier. ALL RIGHTS RESERVED.]

if MEM[PC]==J immediate26

PC = { PC[31:28], immediate26, 2'b00 }

What about JR, JAL?

Aside: MIPS & RISC-V Cheat Sheets

נמצאים במודל

http://www.ece.cmu.edu/~ece447/s15/lib/exe/fetch.php?media=mips_reference_data.pdf

Pseudo Instructions

- abs
- blt
- bgt
- ble
- neg
- not
- bge
- li
- la
- move
- sge
- sgt

MIPS Reference Data				ARITHMETIC CORE INSTRUCTION SET			
CORE INSTRUCTION SET				OPCODE / FMAT / FUNCT			
NAME, MNEMONIC	FOR- MAT	OPERATION (in Verilog)	OPCODE / FUNCT	NAME, MNEMONIC	FOR- MAT	OPERATION	OPCODE / FMAT / FUNCT
Add	add R	R[rd] = R[rs] + R[rt]	(1) 0/20 _{hex}	Branch On FP True	bfc1	IF (FPCond) PC ← PC+4+BranchAddr (4)	11/8/1~
Add Immediate	addi R	R[rd] = R[rs] + SignExtImm	(1,2) 8 _{hex}	Branch On FP False	bfc1f	IF (FPCond) PC ← PC+4+BranchAddr (4)	11/8/0~
Add Unsigned	addiu I	R[rd] = R[rs] + SignExtImm	(2) 9 _{hex}	Divide	div R	Lo ← R[rs] R[rt]; Hi ← R[rs] R[rt]	0~0~1a
And	and R	R[rd] = R[rs] & R[rt]	0/24 _{hex}	Divide Unsigned	divu R	Lo ← R[rs] R[rt]; Hi ← R[rs] R[rt]	(6) 0~0~1b
And Immediate	andi R	R[rd] = R[rs] & ZeroExtImm	(3) 9 _{hex}	FP Add Single	add.s F	F[fd] ← F[fs] + F[ft]	11/10~0
Branch On Equal	beq I	if (R[rs] == R[rt]) PC ← PC+4+BranchAddr	(4) 4 _{hex}	FP Add Double	add.d F	F[fd] ← F[fs] + F[ft]	11/11~0
Branch On Not Equal	bne I	if (R[rs] != R[rt]) PC ← PC+4+BranchAddr	(4) 5 _{hex}	FP Compare Single	c.s F	FPCond ← (F[fs] op F[ft]) ? 1 : 0	11/10~0y
Jump	j J	PC ← JumpAddr	(5) 2 _{hex}	FP Compare Double	c.d F	FPCond ← ((F[fs] op F[ft]) ? 1 : 0)	11/11~0y
Jump And Link	jal J	R[31] ← PC+8; PC ← JumpAddr	(5) 3 _{hex}	FP Divide Single	div.s F	F[fd] ← F[fs] / F[ft]	11/10~0z
Jump Register	jr R	PC ← R[rs]	0/08 _{hex}	FP Divide Double	div.d F	F[fd] ← F[fs] / F[ft]	11/11~0z
Load Byte Unsigned	lbu I	R[rd] = (24'b0, M[R[rs]])	(2) 24 _{hex}	FP Multiply Single	mul.s F	F[fd] ← F[fs] * F[ft]	11/10~0z
Load Halfword	lhu I	R[rd] = (16'b0, M[R[rs]])	(2) 25 _{hex}	FP Multiply Double	mul.d F	F[fd] ← F[fs] * F[ft]	11/11~0z
Load Linked	ll I	R[rd] = M[R[rs]] & SignExtImm	(2,7) 30 _{hex}	FP Subtract Single	sub.s F	F[fd] ← F[fs] - F[ft]	11/10~0z
Load Upper Imm.	lui I	R[rd] = (imm, 16'b0)	(2) 26 _{hex}	FP Subtract Double	sub.d F	F[fd] ← F[fs] - F[ft]	11/11~0z
Load Word	lw I	R[rd] = M[R[rs]] & SignExtImm	(2) 23 _{hex}	FP Subtract Single	sub.s F	F[fd] ← F[fs] - F[ft]	11/10~0z
Nor	nor R	R[rd] = ~(R[rs] & R[rt])	0/27 _{hex}	FP Subtract Double	sub.d F	F[fd] ← F[fs] - F[ft]	11/11~0z
Or	or R	R[rd] = R[rs] R[rt]	0/27 _{hex}	FP Single	lwe1 I	F[rt] ← M[R[rs]] & SignExtImm	(2) 31 _{hex}
Or Immediate	ori I	R[rd] = R[rs] ZeroExtImm	(3) 4 _{hex}	FP Double	lwe1	F[rt] ← M[R[rs]] & SignExtImm	(2) 35 _{hex}
Set Less Than	slt R	R[rd] = (R[rs] < R[rt]) ? 1 : 0	0/24 _{hex}	FP Single	lwe1	F[rt] ← M[R[rs]] & SignExtImm	(2) 35 _{hex}
Set Less Than Imm.	slti I	R[rd] = (R[rs] < SignExtImm) ? 1 : 0	(2) 4 _{hex}	FP Double	lwe1	F[rt] ← M[R[rs]] & SignExtImm	(2) 35 _{hex}
Set Less Than Imm.	sltiu I	R[rd] = (R[rs] < SignExtImm) ? 1 : 0	(2,6) 4 _{hex}	FP Single	lwe1	F[rt] ← M[R[rs]] & SignExtImm	(2) 35 _{hex}
Shift Left Logical	sll R	R[rd] = R[rs] << shamt	0/00 _{hex}	FP Double	lwe1	F[rt] ← M[R[rs]] & SignExtImm	(2) 35 _{hex}
Shift Right Logical	srl R	R[rd] = R[rs] >> shamt	0/02 _{hex}	FP Single	lwe1	F[rt] ← M[R[rs]] & SignExtImm	(2) 35 _{hex}
Store Byte	sb I	M[R[rs]] ← SignExtImm(7:0)	(2) 28 _{hex}	FP Double	lwe1	F[rt] ← M[R[rs]] & SignExtImm	(2) 35 _{hex}
Store Conditional	sc I	M[R[rs]] ← SignExtImm(7:0); R[rt] ← (atomic) ? 1 : 0	(2,7) 38 _{hex}	FP Single	lwe1	F[rt] ← M[R[rs]] & SignExtImm	(2) 35 _{hex}
Store Halfword	sh I	M[R[rs]] ← SignExtImm(15:0)	(2) 29 _{hex}	FP Double	lwe1	F[rt] ← M[R[rs]] & SignExtImm	(2) 35 _{hex}
Store Word	sw I	M[R[rs]] ← SignExtImm(31:0)	(2) 24 _{hex}	FP Single	lwe1	F[rt] ← M[R[rs]] & SignExtImm	(2) 35 _{hex}
Subtract	sub R	R[rd] = R[rs] - R[rt]	(1) 0/22 _{hex}	FP Double	lwe1	F[rt] ← M[R[rs]] & SignExtImm	(2) 35 _{hex}
Subtract Unsigned	subu R	R[rd] = R[rs] - R[rt]	0/23 _{hex}	FP Single	lwe1	F[rt] ← M[R[rs]] & SignExtImm	(2) 35 _{hex}
(1) May cause overflow exception (2) ZeroExtImm = {16(15:0), immediate} (3) ZeroExtImm = {16(15:0), immediate} (4) BranchAddr = {14(immediate)(15), immediate, 2'b0} (5) JumpAddr = {PC+4(31:28), address, 2'b0} (6) Operands considered unsigned numbers (vs. 2's comp.) (7) Atomic test-and-set; R[rt] = 1 if pair atomic, 0 if not atomic				FLOATING-POINT INSTRUCTION FORMATS			
BASIC INSTRUCTION FORMATS				PSEUDOINSTRUCTION SET			
R	opcode	rs	rt	rd	shamt	func1	
I	opcode	rs	rt			immediate	
J	opcode				address		
REGISTER NAME, NUMBER, USE, CALL CONVENTION				REGISTER NAME, NUMBER, USE, CALL CONVENTION			
NAME	NUMBER	USE	PRESERVED/CROSS CALL?	NAME	NUMBER	USE	PRESERVED/CROSS CALL?
\$zero	0	The Constant Value 0	N.A.	\$zero	0	The Constant Value 0	N.A.
\$at	1	Assembler Temporary	No	\$at	1	Assembler Temporary	No
\$v0-\$v1	2-3	Values for Function Results and Expression Evaluation	No	\$v0-\$v1	2-3	Values for Function Results and Expression Evaluation	No
\$a0-\$a7	4-7	Arguments	No	\$a0-\$a7	4-7	Arguments	No
\$t0-\$t7	8-15	Temporaries	No	\$t0-\$t7	8-15	Temporaries	No
\$s0-\$s7	16-23	Saved Temporaries	Yes	\$s0-\$s7	16-23	Saved Temporaries	Yes
\$t8-\$t9	24-25	Temporaries	No	\$t8-\$t9	24-25	Temporaries	No
\$k0-\$k1	26-27	Reserved for OS Kernel	No	\$k0-\$k1	26-27	Reserved for OS Kernel	No
\$gp	28	Global Pointer	Yes	\$gp	28	Global Pointer	Yes
\$sp	29	Stack Pointer	Yes	\$sp	29	Stack Pointer	Yes
\$fp	30	Frame Pointer	Yes	\$fp	30	Frame Pointer	Yes
\$ra	31	Return Address	Yes	\$ra	31	Return Address	Yes


Free & Open RISC-V Reference Card										1					
Base Integer Instructions: RV32I, RV64I, and RV128I							RV Privileged Instructions								
Category	Name	Fmt	RV32I Base			+RV64I, 128	Category	Name	Fmt	RV mnemonic					
Loads	Load Byte	I	LB rd, rs1, imm				CSR Access	Atomic R/W	I	CSROR rd, csr, rs1					
	Load Halfword	I	LH rd, rs1, imm					Atomic Read & Set Bit	I	CSROR rd, csr, rs1					
	Load Word	I	LD rd, rs1, imm					Atomic Read & Clear Bit	I	CSRRC rd, csr, rs1					
	Load Byte Unsigned	I	LBU rd, rs1, imm					Atomic R/W Imm	I	CSRRIW rd, csr, imm					
	Load Half Unsigned	I	LHU rd, rs1, imm					Atomic Read & Set Bit Imm	I	CSRRI rd, csr, imm					
Stores	Store Byte	S	SB rs1, rs2, imm				Atomic Read & Clear Bit Imm	I	CSRRCI rd, csr, imm						
	Store Halfword	S	SH rs1, rs2, imm												
	Store Word	S	SW rs1, rs2, imm												
Shifts	Shift Left	R	SLL rd, rs1, rs2				Change Level	Env. CALL	I	ECALL					
	Shift Left Immediate	I	SLLI rd, rs1, shamt					Environment Breakpoint	I	EBREAK					
	Shift Right	R	SRL rd, rs1, rs2					Environment Return	I	ERET					
	Shift Right Immediate	I	SRLI rd, rs1, shamt					Trap Redirect to Supervisor	I	ERTS					
	Shift Right Arithmetic	R	SRA rd, rs1, rs2					Redirect Trap to Hypervisor	I	HRTH					
Arithmetic	Shift Right Arithmetic	R	SRAI rd, rs1, shamt				Interrupt	Hypervisor Trap to Supervisor	I	WFTS					
	ADD	R	ADD rd, rs1, rs2					Wait for Interrupt	I	WFI					
	ADD Immediate	I	ADDI rd, rs1, imm					MMU	Supervisor FENCE	I	SFENCE.VM rs1				
	SUBTRACT	R	SUB rd, rs1, rs2												
	Load Upper Imm to PC	I	UIPC rd, imm												
Logical	XOR	R	XOR rd, rs1, rs2				Optional Compressed (16-bit) Instruction Extension: RVC								
	XOR Immediate	I	XORI rd, rs1, imm				Category	Name	Fmt	RVC					
	OR	R	OR rd, rs1, rs2				Loads	Load Word	I	LD rd, rs1, 'rs1', imm					
	OR Immediate	I	ORI rd, rs1, imm					Load Word SP	I	LD rd, 'sp', imm*4					
	AND	R	AND rd, rs1, rs2					Load Double	I	LD rd, 'rd', 'rs1', imm*8					
Compare	AND Immediate	I	ANDI rd, rs1, imm					Load Double SP	I	LD rd, 'sp', imm*8					
	Set < rs1, rs2	I	SLT rd, rs1, rs2					Load Quad	I	LD rd, 'rd', 'rs1', imm*16					
	Set < Immediate	I	SLTI rd, rs1, imm					Load Quad SP	I	LD rd, 'sp', imm*16					
	Set < Unsigned	R	SLTU rd, rs1, rs2				Stores	Store Word	C	SW rs1, 'rs2', 'imm*4					
	Set < Imm Unsigned	I	SLTIU rd, rs1, imm						Store Word SP	C	SW rs2, 'sp', imm*4				
Branches	Branch <=	S	BLE rs1, rs2, imm						Store Double	C	SD rs1, 'rs2', 'imm*8				
	Branch <=	S	BLE rs1, rs2, imm						Store Double SP	C	SD rs2, 'sp', imm*8				
	Branch <=	S	BLE rs1, rs2, imm						Store Quad	C	SQ rs1, 'rs2', 'imm*16				
	Branch <=	S	BLE rs1, rs2, imm					Store Quad SP	C	SQ rs2, 'sp', imm*16					
	Branch <=	S	BLE rs1, rs2, imm				Arithmetic	ADD	R	ADD rd, rs1, rs2					
Jump & Link	Branch <=	S	BLE rs1, rs2, imm						ADD Word	R	ADDW rd, rs1				
	Jump & Link Register	J	JAL rd, rs1, imm						ADD Immediate	C	ADDI rd, rs1, imm				
	Synch thread	I	FENCE						ADD Word Imm	C	ADDIW rd, rs1, imm				
	Synch Inst & Data	I	FENCE.I						ADD SP Imm + 4	C	ADDISP rs1, imm*4				
	System	System CALL	I	SCALL					LD	C	LD rd, rs1, imm				
System BREAK		I	SBREAK					LDUI	C	LDUI rd, rs1, imm					
Counters		Read CYCLE	I	RDYCYCLE rd					LDUI rd, rs1, x0	C	LDUI rd, rs1, x0				
Read CYCLE upper Half		I	RDYCYCLEH rd						LDUI rd, rs1, x0	C	LDUI rd, rs1, x0				
Read TIME		I	RDYTIME rd						LDUI rd, rs1, x0	C	LDUI rd, rs1, x0				
Shifts	Read Time Upper Half	I	RDYTIMEH rd						LDUI rd, rs1, x0	C	LDUI rd, rs1, x0				
	Read INST RETIRED	I	RDYINSTRET rd						LDUI rd, rs1, x0	C	LDUI rd, rs1, x0				
	Read INST RETIRED	I	RDYINSTRET rd						LDUI rd, rs1, x0	C	LDUI rd, rs1, x0				
	Branches	Branch <=	S	BLE rs1, rs2, imm						LDUI rd, rs1, x0	C	LDUI rd, rs1, x0			
		Branch <=	S	BLE rs1, rs2, imm						LDUI rd, rs1, x0	C	LDUI rd, rs1, x0			
Branch <=		S	BLE rs1, rs2, imm						LDUI rd, rs1, x0	C	LDUI rd, rs1, x0				
Branch <=		S	BLE rs1, rs2, imm						LDUI rd, rs1, x0	C	LDUI rd, rs1, x0				
Branch <=		S	BLE rs1, rs2, imm						LDUI rd, rs1, x0	C	LDUI rd, rs1, x0				
Jump	Jump Register	C	J rd, rs1, imm						LDUI rd, rs1, x0	C	LDUI rd, rs1, x0				
	Jump Register	C	J rd, rs1, imm						LDUI rd, rs1, x0	C	LDUI rd, rs1, x0				
	Jump Register	C	J rd, rs1, imm						LDUI rd, rs1, x0	C	LDUI rd, rs1, x0				
	Jump Register	C	J rd, rs1, imm						LDUI rd, rs1, x0	C	LDUI rd, rs1, x0				
	Jump Register	C	J rd, rs1, imm						LDUI rd, rs1, x0	C	LDUI rd, rs1, x0				
System Env. BREAK	System Env. BREAK	I	SBREAK						LDUI rd, rs1, x0	C	LDUI rd, rs1, x0				
	System Env. BREAK	I	SBREAK						LDUI rd, rs1, x0	C	LDUI rd, rs1, x0				
	System Env. BREAK	I	SBREAK						LDUI rd, rs1, x0	C	LDUI rd, rs1, x0				
	System Env. BREAK	I	SBREAK						LDUI rd, rs1, x0	C	LDUI rd, rs1, x0				
	System Env. BREAK	I	SBREAK						LDUI rd, rs1, x0	C	LDUI rd, rs1, x0				
32-bit Instruction Formats							16-bit (RVC) Instruction Formats								
I	31	30	25-24	23	21-20	19-14	12	11	6	5	4	3	2	1	0
R	funct7			rs2		rs1		funct3					rs2		
I			imm[11:0]			rs1		funct3					rs1		
S				rs2		rs1		funct3					rs2		
SB			imm[11:0]			rs1		funct3					rs1		
U			imm[31:25]			rs1		funct3					rs2		
				rs2		rs1		funct3					rs1		
						rs1		funct3					rs2		
						rs1		funct3					rs1		
						rs1		funct3					rs2		
						rs1		funct3					rs1		
						rs1		funct3					rs2		
						rs1		funct3					rs1		
						rs1		funct3					rs2		
						rs1		funct3					rs1		

Conditional Branch Instructions (MIPS)

- Assembly (e.g., branch if equal)

BEQ rs_{reg} rt_{reg} $immediate_{16}$

- Machine encoding

 

I-type

- Semantics (assuming no branch delay slot)

if $MEM[PC] == BEQ\ rs\ rt\ immediate_{16}$

target = $PC + 4 + \text{sign-extend}(immediate) \times 4$


! פעולת השוואה נעשית ב-ALU

if $GPR[rs] == GPR[rt]$ then PC $\rightarrow$ target

else PC $\rightarrow$ PC + 4


Conditional Branch Datapath (for you to finish)

פתרון בשקף הבא...

 

Conditional Branch Datapath (finished :-)

 
כאשר מוסיפים תמיכה בהסתעפות
מותנה יש צורך לבטל את החיבור
שמשמאל (מסומן בשני קווים
אלכסוניים)



**Based on original figure from [P&H CO&D, COPYRIGHT 2004 Elsevier, ALL RIGHTS RESERVED.]


We need a second adder, since the ALU is already doing subtraction for the beq.

GUY

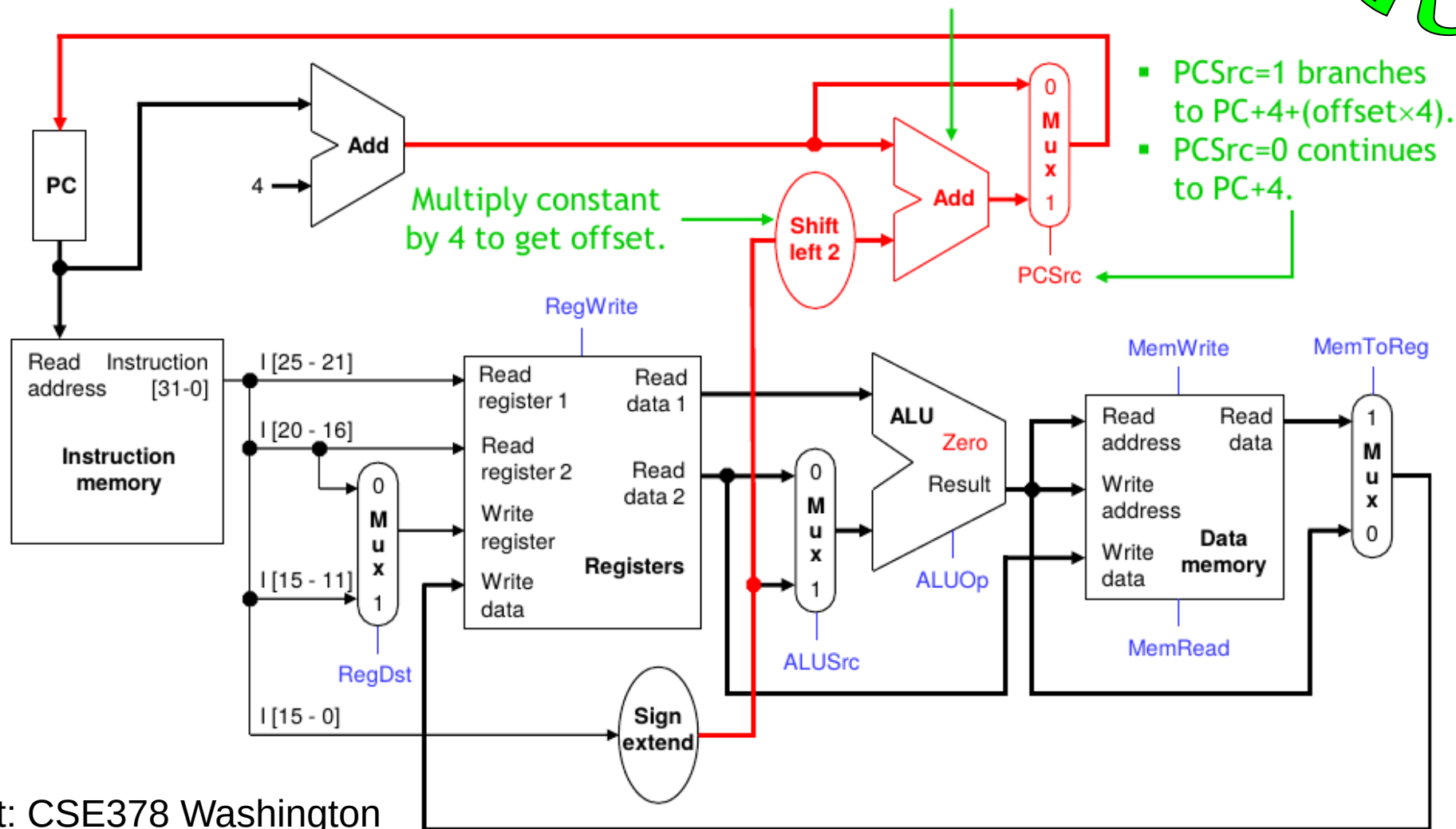


The Final Datapath (without the controls)

GUY

 


ניתן לצייר
על שקף
זה

 

H&P CO&D

FIGURE 4.24 The simple control and datapath are extended to handle the **jump** instruction. An additional multiplexor (at the upper right) is used to choose between the jump target and either the branch target or the sequential instruction following this one. This multiplexor is controlled by the jump control signal. The jump target address is obtained by shifting the lower 26 bits of the jump instruction left 2 bits, effectively adding 00 as the low-order bits, and then concatenating the upper 4 bits of PC + 4 as the high-order bits, thus yielding a 32-bit address.


Putting It All Together (MIPS)

 

Single-Cycle Control Logic

Control

 התרשים כאן מחדד את קווי הבקרה אך הוא חלקי (אין כאן תמיכה מלאה בכל ההוראות)



1- will connect sext(imm) to the ALU B input [in lw or sw inst.]

MemRead – **0** - nothing happens. **1**- data is read from M[ALU output]

MemWrite – **0** - nothing happens. **1**- GPR[Rt] is written into M[ALU output] at the next rising edge of the CK




1 – if we do write back to GPR [Rtype, lw]

MemToReg – 0 – The ALU output is fed to the GPR Write Data input [Rtype]. **1**- Data read from Memory is fed to the GPR Write Data input [lw]

RegDst – 0 – The GPR Write Reg gets Rt field of the instruction [lw]. **1**– The GPR Write Reg gets Rd field of instruction [Rtype]

 Branch – 0 – ia all instructions except beq. **1**- in beq. Selects whether to branch or not.



Control


We would like to build the Control Decoder together

Instr.	ALU Src	ALUOp [1:0]		Mem Read	Mem Write	Mem Reg	Reg Dst	Reg Write	Branch
R-type									
lw									
sw									
beq									

We can fill up columns


We only read from memory in lw instruction, so

 We only write to memory in sw instruction, so



Instr.	ALU Src	ALUOp [1:0]	Mem Read	Mem Write	Mem Reg	Reg Dst	Reg Write	Branch
R-type			0	0				
lw			1	0				
sw			0	1				
beq			0	0				

 A better way is to follow
Each instruction and see
What happens in the
Data-Path during the
Execution of the instruction



In Rtype we use $GPR[Rs]$ op $GPR[Rt]$

Thus, $ALUSrc = 0$

In Rtype we must have $ALUOp = 10$ (function)

$MemRead = 0$ and $MemWrite = 0$

$MemToReg = 0$

Instr.	ALUSrc	ALUOp [1:0]	MemRead	MemWrite	MemReg	RegDst	RegWrite	Branch
R-type	0	1 0	0	0	0	1	1	0
lw			1	0				
sw			0	1				
hsw			0	0				


$RegDst = 1$ to select Rd

$RegWrite = 1$ to write to the GPR

$Branch = 0$ so we always get
 $PC = PC + 4$

LW

אנימציה

 

In lw we use $GPR[Rs] + sext(imm)$

Thus, $ALUSrc = 1$

In lw we must have $ALUSOP = 00$ (add)

$MemRead = 1$ and $MemWrite = 0$

$MemToReg = 1$

Instr.	ALUSrc	ALUOp [1:0]	MemRead	MemWrite	MemReg	RegDst	RegWrite	Branch
R-type	0	1 0	0	0	0	1	1	0
lw	1	0 0	1	0	1	0	1	0
sw			0	1				
			0	0				
beq								


$RegDst = 0$ to select Rt

$RegWrite = 1$ to write to the GPR

Branch=0 so we always get

$PC = PC + 4$

SW

 

Thus, ALUSrc =1

In sw we must have $ALUSOP = 00$ (add)

MemRead=0 and MemWrite=1

MemToReg=X. We do not write back!

Instr.	ALU Src	ALUOp [1:0]		Mem Read	Mem Write	Mem Reg	Reg Dst	Reg Write	Branch
R-type	0	1	0	0	0	0	1	1	0
lw	1	0	0	1	0	1	0	1	0
sw	1	0	0	0	1	X	X	0	0
beq				0	0				

RegDst=X. We do not write back!

RegWrite=0. We do not write back!

Branch=0 so we always get

PC=PC+4

Beq

Zero=1 if
ALU output
is 000...000
else Zero=0


In beq we use $GPR[R_s] - GPR[R_t]$

Thus, $ALUSrc = 0$

In beq we subtract so $ALUSOP = 01$ (sub)

$MemRead=0$ and $MemWrite=0$

$MemToReg=X$. We do not write back!

 

Instr.	ALUSrc	ALUOp [1:0]	MemRead	MemWrite	MemToReg	RegDst	RegWrite	Branch
R-type	0	1	0	0	0	1	1	0
lw	1	0	0	1	0	1	1	0
sw	1	0	0	1	X	X	0	0
beq	0	0	1	0	0	X	0	1


$RegDst=X$. We do not write back!

$RegWrite=0$ We do not write back!

Branch=1 so we check Zero to

decide whether to
branch ($PC = \text{branch target}$)


or not to branch ($PC = PC + 4$)

 

So the final Control Decoder is as follows:


Instr.	ALU Src	ALUOp [1:0]	Mem Read	Mem Write	Mem Reg	Reg Dst	Reg Write	Branch
R-type	0	1 0	0	0	0	1	1	0
lw	1	0 0	1	0	1	0	1	0
sw	1	0 0	0	1	X	X	0	0
beq	0	0 1	0	0	X	X	0	1

Inputs

 

Control Decoder


Outputs

 

Instr.	ALU Src	ALUOp [1:0]		Mem Read	Mem Write	Mem Reg	Reg Dst	Reg Write	Branch
R-type	0	1	0	0	0	0	1	1	0
lw	1	0	0	1	0	1	0	1	0
sw	1	0	0	0	1	X	X	0	0
beq	0	0	1	0	0	X	X	0	1

Single-Cycle Hardwired Control (MIPS)

 - As combinational function of $\text{Inst} = \text{MEM}[\text{PC}]$




R-type

I-type

J-type

- Consider – סט מצומצם
 - All R-type and I-type ALU instructions
 - LW and SW
 - BEQ, BNE, BLEZ, BGTZ
 - L, LR, LAL, LALR

Putting It All Together (MIPS)

 

Single-Bit Control Signals

	When De-asserted	When asserted	Equation
RegDest	GPR write select according to rt, i.e., inst[20:16]	GPR write select according to rd, i.e., inst[15:11]	$opcode == 0$
ALUSrc	2 nd ALU input from 2 nd GPR read port	2 nd ALU input from sign-extended 16-bit immediate	$(opcode \neq 0) \ \&\&$ $(opcode \neq BEQ) \ \&\&$

JAL and JALR require additional RegDest and MemtoReg options

Single-Bit Control Signals

	When De-asserted	When asserted	Equation
MemRead	Memory read disabled	Memory read port return load value	<code>opcode==LW</code>
MemWrite	Memory write disabled	Memory write enabled	<code>opcode==SW</code>
PCSrc ₁	According to PCSrc ₂	next PC is based on 26-bit immediate jump target	<code>(opcode==J) </code> <code>(opcode==JAL)</code>
PCSrc ₂	next PC = PC + 4	next PC is based on 16-bit immediate branch target	<code>(opcode==Bxx) &&</code> "bcond is satisfied"

ALU Control

אנימציה

case opcode

R-type: '0' ^ select operation according to funct

'ALUi' ^ selection operation according to opcode

'LW' ^ select addition

'SW' ^ select addition

'Bxx' ^ select bcond generation function

other inst. ^ don't care

Example of ALU CMD (operations)


ADD, SUB, AND, OR, XOR, NOR, etc.

bcond on equal, not equal, LE zero, GT zero, etc.

Instr.	ALUOp [1:0]	
R-type	1	0
lw	0	0
sw	0	0
beq	0	1

Func.

ALUOP

 


ALU CMD

MIPS ALU CMDs

- Here's a simple ALU with five operations, selected by a 3-bit control signal ALU CMD

ALU CMD	Function
000	and
001	or
010	add
110	subtract
111	slt

 

CORE INSTRUCTION SET

NAME, MNEMONIC	FOR-MAT	OPERATION (in Verilog)	OPCODE / FUNCT (Hex)
Add	add R	$R[rd] = R[rs] + R[rt]$	(1) 0 / 20 _{hex}


Taken from: CSE378 University of Washington

<https://courses.cs.washington.edu/courses/cse378/10sp/lectures.html>

מתוך דפי הסיכום של MIPS:

 Example: ALU Design – The Logic part


- ALU operation ($F_{2:0}$) comes from the control logic




$F_{2:0}$	Function
000	A & B
001	A B
010	A + B
011	not used
100	A & $\sim B$
101	A $\sim B$
110	A - B
111	SLT




I-Type ALU

 

 
**Based on original figure from [P&H CO&D, COPYRIGHT 2004
Elsevier. ALL RIGHTS RESERVED.]



 


Branch (Not Taken)

 Some control signals are dependent on the processing of data




Branch (Taken)

 Some control signals are dependent on the processing of data



**Based on original figure from [P&H CO&D, COPYRIGHT 2004 Elsevier. ALL RIGHTS RESERVED.]

Jump

 

**Based on original figure from [P&H CO&D, COPYRIGHT 2004 Elsevier. ALL RIGHTS RESERVED.]

What is in That Control Box?

- Combinational Logic ✉ **Hardwired Control**
 - Idea: Control signals generated combinatorially based on instruction
 - Necessary in a single-cycle microarchitecture...
- Sequential Logic ✉ **Sequential/Microprogrammed Control**
 - Idea: A memory structure contains the control signals associated with an instruction
יוסבר במצגת נפרדת!
 - Control Store

Evaluating the Single-Cycle Microarchitecture

A Single-Cycle Microarchitecture

- Is *this* a good idea/design?
- When is this a good design?
- When is this a bad design?
- How can we design a better microarchitecture?



A Single-Cycle Microarchitecture: Analysis

- Every instruction takes 1 cycle to execute
 - CPI (Cycles per instruction) is strictly 1
- How long each instruction takes is determined by **how long the slowest instruction takes to execute**
 - **Even though many instructions do not need that long to execute**
- Clock cycle time of the microarchitecture is determined by how long it takes to complete the slowest instruction
 - **Critical path** of the design is determined by the processing time of the slowest instruction


What is the Slowest Instruction to Process?

- Let's go back to the basics
- All five phases of the instruction processing cycle take a *single machine clock cycle* to complete
 1. Instruction fetch (IF)
 2. Instruction decode and register operand fetch (ID/RF)
 3. Execute/Evaluate memory address (EX/AG)
 4. Memory operand fetch (MEM)
 5. Store/writeback result (WB)
- Do each of the above phases take the same time (latency) for all instructions?
 - לא כל ההוראות צריכות את כל 5 השלבים.
 - לא כל שלב אורך אותו הזמן.
 - סביר שהפקודה האיטית ביותר תזדקק לכל השלבים.


דוגמה - Single-Cycle Datapath Analysis

- Assume – זוהי רק דוגמה המניחה ערכים להשעיות בכל אחד מהשלבים
 - ❑ memory units (read or write): 200 ps
 - ❑ ALU and adders: 100 ps
 - ❑ register file (read or write): 50 ps
 - ❑ other combinational logic: 0 ps
 - ❑ בשקף הבא נציב את הזמנים ונחפש את ההוראה הכי איטית

steps	IF	ID	EX	MEM	WB	Delay
resources	mem	RF	ALU	mem	RF	
R-type	200	50	100		50	400
I-type	200	50	100		50	400
LW	200	50	100	200	50	600
SW	200	50	100	200		550
Branch	200	50	100			350
Jump	200					200

 



Let's Find the Critical Path

 


R-Type and I-Type ALU → critical path


אנימציה

 

 


 

Branch Taken

 

Jump

 

What About Control Logic?

עד עכשיו הנחנו עיכובים רק בגלל ה- datapath מה קורה עם עיכובים בצד של הבקרה?

- How does that affect the critical path?
- Food for thought for you:
 - Can control logic be on the critical path? (*)
 - A note on CDC 5600: control store access too long.




(*) בהחלט כן. ראו לפני 2 שקפים עבור Branch Taken. אותות הבקרה תלויים בנתונים ונוצרות השהיות. דוגמה נוספת: אותות הבקרה שקשורים ב- cache hit/miss נמצאים על הנתיב הקריטי.

(**) Seymour Cray היה המהנדס הראשי ב-CDC. הוא ואנשיו קיצרו את ה- pipeline כדי להתגבר על בעיית זמן הגישה הארוך



What is the Slowest Instruction to Process? :ר"א

 - Memory is not “magic”
- What if memory *sometimes* takes 100ms to access?
- Does it make sense to have a simple register to register add or jump to take {100ms+all else to do a memory operation}?
- And, what if you need to access memory more than once to process an instruction?
 - Which instructions need this?
 - Do you provide multiple ports to memory?



Single Cycle μ Arch: Complexity

- Contrived (=מועסקים)
 - All instructions run as slow as the slowest instruction
- Inefficient
 - All instructions run as slow as the slowest instruction
 - Need to replicate a resource if it is needed more than once by an instruction during different parts of the instruction processing cycle
- Not necessarily the simplest way to implement an ISA
 - Single-cycle implementation of REP MOVSB (x86) or INDEX (VAX)?
- Not easy to optimize/improve performance
 - Optimizing the common case does not work (e.g. common instructions)
 - Need to optimize the worst case all the time

(Micro)architecture Design Principles


■ Critical path design (Guy: optimize for performance)

- Find and **decrease** the maximum **combinational logic delay**
- Break a path into multiple cycles if it takes too long

למרות הרצון לאופטימיזציה של
הנתיב הקריטי כדי שנוכל
להעלות את התדר, לא תמיד
הדבר רצוי בגלל צריכת ההספק

■ Bread and butter (common case) design

 - Spend time and resources on where it matters most
 - i.e., improve what the machine is really designed to
- **Common case vs. uncommon case**



P is proportional to f^3

■ Balanced design

- **Balance** instruction/data flow through hardware components
- **Design to eliminate bottlenecks**: balance the hardware for the work

Single-Cycle Design vs. Design Principles

אנימציה

- Critical path design
- Bread and butter (common case) design
- Balanced design

How does a single-cycle microarchitecture fare in light of these principles?

Aside: System Design Principles

- When designing computer systems/architectures, it is important to follow good principles
- “principled design”

Frank Lloyd Wright: “architecture [...] based upon **principle, and not upon **precedent**”** = אדריכלות המבוססת על עיקרון, ולא על תקדים

Guy: **Patterson and Hennessy design principles:**

- (1) Simplicity favors regularity;
- (2) Make the common case fast;
- (3) Smaller is faster;
- (4) Good design demands good compromises;

Frank Lloyd Wright


- “architecture [...] based upon **principle**, and not upon **precedent**”



Aside: System Design Principles

- We will continue to cover key principles in this course
- Here are some references where you can learn more
- Yale Patt, "Requirements, Bottlenecks, and Good Fortune: Agents for Microprocessor Evolution," Proc. of IEEE, 2001. (Levels of transformation, design point, etc)
- Mike Flynn, "Very High-Speed Computing Systems," Proc. of IEEE, 1966. (Flynn's Bottleneck ➡ Balanced design)
- Gene M. Amdahl, "Validity of the single processor approach to achieving large scale computing capabilities", AFIPS Conference, April 1967. (Amdahl's Law ➡ Common-case design)
- Butler W. Lampson, "Hints for Computer System Design," ACM Operating Systems Review, 1983.


Aside: One Important Principle

 



- Keep it simple
- “Everything should be made as simple as possible, but no simpler.”
 - Albert Einstein
- And, do not forget: “An engineer is a person who can do for a dime what any fool can do for a dollar.”

הציטוט המדויק:

 
An engineer can do for a dollar“
"what any fool can do for two



Single Cycle MCU Examples

  

Intel 8051 Microarchitecture

 



Single Cycle 8051 Core—AT89LP Family of High Performance & Low Power Flash Microcontrollers

By David Lee, Marketing Manager
&
Ben Froemming, Design Manager

Summary

The Atmel AT89LP family of products features a single-cycle 8051 core within a highly integrated microcontroller allowing designers to achieve 6x to 12x more performance compared to classic 8051 devices. The 8051 architecture has been used in the industry for decades and remains very popular with system developers. AT89LP microcontrollers offer full binary code compatibility with the original MSC®51 instruction set, ensuring an easy migration path. The single-cycle core provides designers a unique opportunity to upgrade their application with more performance (up to 20 MIPS), less power consumption (up to 80% savings) and code size ranging from 2KB to 64KB. AT89LP microcontrollers reduce system cost and enable faster time-to-market by integrating more system features on chip.

Reference:
[https://
ww1.microchip.com/
downloads/en/
DeviceDoc/
doc4088.pdf](https://ww1.microchip.com/downloads/en/DeviceDoc/doc4088.pdf)



MicroConverter® Multichannel 24-/16-Bit ADCs with Embedded 62 kB Flash and Single-Cycle MCU



Data Sheet

ADuC845/ADuC847/ADuC848

FEATURES

- High resolution Σ - Δ ADCs
- 2 independent 24-bit ADCs on the **ADuC845**
- Single 24-bit ADC on the **ADuC847** and
single 16-bit ADC on the **ADuC848**
- Up to 10 ADC input channels on all devices
- 24-bit no missing codes
- 22-bit rms (19.5 bit p-p) effective resolution
- Offset drift 10 nV/°C, gain drift 0.5 ppm/°C chop enabled

Memory

- 62-kbyte on-chip Flash/EE program memory
- 4-kbyte on-chip Flash/EE data memory
- Flash/EE, 100-year retention, 100 kcycle endurance
- 3 levels of Flash/EE program memory security
- In-circuit serial download (no external hardware)
- High speed user download (5 sec)
- 2304 bytes on-chip data RAM

8051-based core

- 8051-compatible instruction set
- High performance single-cycle core
- 32 kHz external crystal
- On-chip programmable PLL (12.58 MHz max)




Power

- Normal: 4.8 mA max at 3.6 V (core CLK = 1.57 MHz)
- Power-down: 20 μ A max with wake-up timer running
- Specified for 3 V and 5 V operation
- Package and temperature range:
- 52-lead MQFP (14 mm $\times$ 14 mm), -40°C to +125°C
- 56-lead LFCSP (8 mm $\times$ 8 mm), -40°C to +85°C

APPLICATIONS


- Multichannel sensor monitoring
- Industrial/environmental instrumentation
- Weigh scales, pressure sensors, temperature monitoring
- Portable instrumentation, battery-powered systems
- Data logging, precision system monitoring

FUNCTIONAL BLOCK DIAGRAM

 

What is C2000?

 The 32-bit real-time microcontroller family



• DSP performance within a Microcontroller architecture

- 40-300MHz C28x CPU
 - Built-in DSP functions
 - Single Cycle 32x32-bit MAC
- Control Law Accelerator
- Floating-Point Unit
- Embedded Flash

• Fine-tuned for real-time control

- Optimized core
- Fast interrupts
- Flexible interrupt system

• Comprehensive Peripheral Set

- Best in class ADC performance
- Flexible high resolution PWMs
- Advanced Capture, Quadrature Encoder Interfaces
- CAN, LIN, SPI, I2C, SCI/UART, McBSP


• Broad portfolio of configurations

- 40-300 MHz
- Fixed and Floating-point devices
- 32-512KB of Flash
- From sub \$2 to \$20


Software compatibility across C2000 family

סיכום - Single Cycle

Single-Cycle μ arch I (H&P 1"פנ) - MIPS

 

 (תצורה מעט שונה עפ"י H&H) Single-Cycle μ arch II



הנושא הבא:

**נעבור עתה לפרק 7 מתוך H&H,
נתמקד במעבד RISC-V ונרחיב
ונעסוק גם ב-**





Multi-Cycle Microarchitectures

**Digital Design &
Computer Architecture**
Sarah Harris & David Harris

**Chapter 7:
Microarchitecture**


Chapter 7 :: Topics

- Introduction
- Performance Analysis
- Single-Cycle Processor
- Multicycle Processor
- Pipelined Processor
- Advanced Microarchitecture

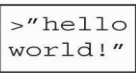   Application Software	
Operating Systems	
Architecture	
Micro-architecture	
Logic	
Digital Circuits	
Analog Circuits	
Devices	
Physics	

Introduction

 - **Microarchitecture:** how to implement an architecture in hardware
- Processor:
 - **Datapath:** functional blocks
 - **Control:** control signals



Microarchitecture

- **Multiple implementations** for a single architecture:
 - **Single-cycle:** Each instruction executes in a single cycle
 - **Multicycle:** Each instruction is broken up into series of shorter steps
 - **Pipelined:** Each instruction broken up into series of steps & multiple instructions execute at once

Processor Performance

- **Program execution time**

Execution Time = (#instructions)(cycles/instruction)(seconds/cycle)

- **Definitions:**

- CPI: Cycles/instruction
- clock period: seconds/cycle
- IPC: instructions/cycle = IPC

- **Challenge is to satisfy constraints of:**

- Cost
- Power
- Performance

RISC-V Processor

- Consider **subset** of RISC-V instructions:
 - R-type ALU instructions:
 - **add, sub, and, or, slt**
 - Memory instructions:
 - **lw, sw**
 - Branch instructions:
 - **beq**


Architectural State Elements

Determines everything about a processor:

- **Architectural state:**

- 32 registers
- PC
- Memory

RISC-V Architectural State Elements

 

Chapter 7: Microarchitecture

Single-Cycle RISC-V Processor

Single-Cycle RISC-V Processor

- Datapath
- Control

Example Program

- Design datapath
- View example program executing


Example Program:

Address	Instruction	Type	Fields						Machine Language
0x1000	L7: lw x6, -4(x9)	I	imm ^{11:0}	rs1	f3	rd	op		
			1111111111100	01001	010	00110	0000011		FFC4A303
0x1004	sw x6, 8(x9)	S	imm ^{11:5}	rs2	rs1	f3	imm ^{4:0}	op	
			00000000 00110	01001	010	01000	0100011		0064A423
0x1008	or x4, x5, x6	R	funct7	rs2	rs1	f3	rd	op	
			00000000 00110	00101	110	00100	0110011		0062E233
0x100C	beq x4, x4, L7	B	imm ^{12,10:5}	rs2	rs1	f3	imm ^{4:1,11}	op	
			11111111 00100	00100	000	10101	1100011		FE420AE3

Single-Cycle RISC-V Processor




- **Datapath:** start with `lw` instruction
- **Example:**
`lw x6, -4(x9)`
`lw rd, imm(rs1)`

I-Type

 

Single-Cycle Datapath: lw fetch


STEP 1: Fetch instruction

   

Address	Instruction	Type	Fields	Machine Language
0x1000	L7: lw x6, -4(x9)	I	imm 11:0 1111111111100 rs1 01001 f3 010 rd 00110 op 0000011	FFC4A303

Single-Cycle Datapath: `lw` Reg Read

 
STEP 2: Read source operand (**rs1**) from RF



Address	Instruction	Type	Fields	Machine Language
0x1000	L7: <code>lw x6, -4(x9)</code>	I	imm_{11:0} 1111111111100 rs1 01001 f3 010 rd 00110 op 0000011	FFC4A303

Single-Cycle Datapath: lw Immediate

STEP 3: Extend the immediate

 


Address	Instruction	Type	Fields	Machine Language
0x1000	L7: lw x6, -4(x9)	I	imm11:0 1111111111100 rs1 01001 f3 010 rd 00110 op 0000011	FFC4A303

Single-Cycle Datapath: lw Address

STEP 4: Compute the memory address


ALUControl 2:0	Function
000	add
001	subtract
010	and
011	or
101	SLT

 

Address	Instruction	Type	Fields	Machine Language
0x1000	L7: lw x6, -4(x9)	I	imm_{11:0} 111111111100 rs1 01001 f3 010 rd 00110 op 0000011	FFC4A303

Single-Cycle Datapath: lw Mem Read

 
STEP 5: Read data from memory and write it back to register file



Address	Instruction	Type	Fields	Machine Language										
0x1000	L7: lw x6, -4(x9)	I	<table><tr><td>imm 11:0</td><td>rs1</td><td>f3</td><td>rd</td><td>op</td></tr><tr><td>111111111100</td><td>01001</td><td>010</td><td>00110</td><td>0000011</td></tr></table>	imm 11:0	rs1	f3	rd	op	111111111100	01001	010	00110	0000011	FFC4A303
imm 11:0	rs1	f3	rd	op										
111111111100	01001	010	00110	0000011										

Single-Cycle Datapath: PC Increment

 STEP 6: Determine address of next instruction




Address	Instruction	Type	Fields	Machine Language
0x1000 18	L7: lw x6, -4(x9)	I	imm 11:0 1111111111100 rs1 01001 f3 010 rd 00110 op 0000011	FFC4A303
Digital Design & Computer Architecture Microarchitecture				

Chapter 7: Microarchitecture

Single-Cycle Datapath: Other Instructions

Single-Cycle Datapath: SW


 
- **Immediate:** now in {instr[31:25], instr[11:7]}
- **Add control signals:** ImmSrc, MemWrite



Address	Instruction	Type	Fields	Machine Language
0x1004	sw x6, 8(x9)	S	imm 11:5 0000000 rs2 00110 rs1 01001 f3 010 imm 4:0 01000 op 0100011	0064A423


Single-Cycle Datapath: Immediate

ImmSrc	ImmExt	Instruction Type
0	{{20{instr[31]}}, instr[31:20] }	I-Type
1	{{20{instr[31]}}, instr[31:25], instr[11:7] }	S-Type

  

Single-Cycle Datapath: R-type

 
- Read from **rs1** and **rs2** (instead of **imm**)
- Write **ALUResult** to **rd**



Address	Instruction	Type	Fields	Machine Language
0x1008	or x4, x5, x6	R	funct7 0000000 rs2 00110 rs1 00101 f3 110 rd 00100 op 0110011	0062E233

Single-Cycle Datapath: beq

 Calculate **target address**: $PCTarget = PC + imm$




Address	Instruction	Type	Fields							Machine Language
0x100C	beq x4, x4, L7	B	imm ^{12,10:5}	rs2	rs1	f3	imm ^{4:1,11}	op	FE420AE3	
23	Digital Design & Computer Architecture				Microarchitecture					


Single-Cycle Datapath: ImmExt

ImmSrc _{1:0}	ImmExt	Instruction Type
00	{{20{instr[31]}}, instr[31:20] }	I-Type
01	{{20{instr[31]}}, instr[31:25], instr[11:7] }	S-Type
10	{{19{instr[31]}}, instr[31], instr[7], instr[30:25], instr[11:8], 1'b0 }	B-Type


I-Type

 


S-Type

 

B-Type

 

Single-Cycle RISC-V Processor

 


Chapter 7: Microarchitecture


Single-Cycle Control

Single-Cycle Control

High-Level View

 


Low-Level View

 


Single-Cycle Control: Main Decoder

op	Instr.	RegWrite	ImmSrc	ALUSrc	MemWrite	ResultSrc	Branch	ALUOp
3	lw							
35	sw							
51	R-type							
99	beq							

 


Review: ALU

ALUControl _{2:0}	Function
000	add
001	subtract
010	and
011	or
101	SLT

 


Review: ALU

ALUControl _{2:0}	Function
000	add
001	subtract
010	and
011	or
101	SLT

 


Single-Cycle Control: ALU Decoder

 


Single-Cycle Control: ALU Decoder

<i>ALUOp</i>	<i>funct3</i>	<i>op</i> ₅ , <i>funct7</i> ₅	Instruction	<i>ALUControl</i> _{2:0}
00	x	x	lw, sw	000 (add)
01	x	x	beq	001 (subtract)
10	000	00, 01, 10	add	000 (add)
	000	11	sub	001 (subtract)
	010	x	slt	101 (set less than)
	110	x	or	011 (or)
	111	x	and	010 (and)

 

Example: and

op	Instruct	RegWrite	ImmSrc	ALUSrc	MemWrite	ResultSrc	Branch	ALUOp
51	R-type	1	XX	0	0	0	0	10

 

and x5, x6, x7

Chapter 7: Microarchitecture

Extending the Single-Cycle Processor

Extended Functionality: I-Type ALU

Enhance the single-cycle processor to handle **I-Type ALU instructions**: `addi`, `andi`, `ori`, and `slti`


- **Similar to R-type** instructions
- But **second source** comes from **immediate**
- Change **ALUSrc** to select the immediate
- And **ImmSrc** to pick the correct immediate

Extended Functionality: I-Type ALU

op	Instruct.	RegWrite	ImmSrc	ALUSrc	MemWrite	ResultSrc	Branch	ALUOp
3	lw	1	00	1	0	1	0	00
35	sw	0	01	1	1	X	0	00
51	R-type	1	XX	0	0	0	0	10
99	beq	0	10	0	0	X	1	01
19	I-type	1	00	1	0	0	0	10

Extended Functionality: addi

op	Instruct.	RegWrite	ImmSrc	ALUSrc	MemWrite	ResultSrc	Branch	ALUOp
19	I-type	1	00	1	0	0	0	10

 


addi x5, x6, -33

Extended Functionality: `jal`

Enhance the single-cycle processor to handle `jal`

- **Similar to `beq`**
- But jump is **always taken**
 - *PCSrc* should be 1
- **Immediate format** is different
 - Need a new *ImmSrc* of 11
- And `jal` must **compute PC+4** and **store in `rd`**
 - Take PC+4 from adder through ResultMux


Extended Functionality: jal

 


Extended Functionality: *ImmExt*

ImmSrc _{1:0}	ImmExt	Instruction Type
00	{{20{instr[31]}}, instr[31:20]}	I-Type
01	{{20{instr[31]}}, instr[31:25], instr[11:7]}	S-Type
10	{{19{instr[31]}}, instr[31], instr[7], instr[30:25], instr[11:8], 1'b0}	B-Type
11	{{12{instr[31]}}, instr[19:12], instr[20], instr[30:21], 1'b0}	J-Type


I-Type

 


B-Type

 

S-Type

 

J-Type

 


Extended Functionality: jal

op	Instruct.	RegWrite	ImmSrc	ALUSrc	MemWrite	ResultSrc	Branch	ALUOp	Jump
3	lw	1	00	1	0	01	0	00	0
35	sw	0	01	1	1	XX	0	00	0
51	R-type	1	XX	0	0	00	0	10	0
99	beq	0	10	0	0	XX	1	01	0
19	I-type	1	00	1	0	00	0	10	0
111	jal	1	11	X	0	10	0	XX	1

Extended Functionality: jal

op	Instruct.	RegWrite	ImmSrc	ALUSrc	MemWrite	ResultSrc	Branch	ALUOp	Jump
111	jal	1	11	X	0	10	0	XX	1

 

Chapter 7: Microarchitecture

Single-Cycle Performance


Processor Performance

Program Execution Time

= (#instructions)(cycles/instruction)(seconds/cycle)

= # instructions x CPI x T_c

Single-Cycle Processor Performance

 

T_C limited by critical path ($1w$)

Single-Cycle Processor Performance

- **Single-cycle critical path:**

$$T_{c_single} = t_{pcq_PC} + t_{mem} + \max[t_{RFread}, t_{dec} + t_{ext} + t_{mux}] + t_{ALU} + t_{mem} + t_{mux} + t_{RFsetup}$$

- **Typically, limiting paths are:**

- memory, ALU, register file

- So,
$$\begin{aligned} T_{c_single} &= t_{pcq_PC} + t_{mem} + t_{RFread} + t_{ALU} + t_{mem} + t_{mux} + t_{RFsetup} \\ &= t_{pcq_PC} + 2t_{mem} + t_{RFread} + t_{ALU} + t_{mux} + t_{RFsetup} \end{aligned}$$

Single-Cycle Performance Example

Element	Parameter	Delay (ps)
Register clock-to-Q	t_{pcq_PC}	40
Register setup	t_{setup}	50
Multiplexer	t_{mux}	30
AND-OR gate	t_{AND-OR}	20
ALU	t_{ALU}	120
Decoder (Control Unit)	t_{dec}	25
Extend unit	t_{ext}	35
Memory read	t_{mem}	200
Register file read	t_{RFread}	100
Register file setup	$t_{RFsetup}$	60

$$T_{C_single} = t_{pcq_PC} + 2t_{mem} + t_{RFread} + t_{ALU} + t_{mux} + t_{RFsetup}$$
$$=$$

Single-Cycle Performance Example

Program with 100 billion instructions:

$$\begin{aligned}\text{Execution Time} &= \# \text{ instructions} \times \text{CPI} \times T_c \\ &= 75 \text{ seconds}\end{aligned}$$

Chapter 7: Microarchitecture

Multicycle RISC-V Processor

Note to self:
For a few additional slides switch to my "old" Muti-cycle presentation

Single- vs. Multicycle Processor

- **Single-cycle:**
 - + simple
 - cycle time limited by longest instruction (lw)
 - separate memories for instruction and data
 - 3 adders/ALUs
- **Multicycle processor** addresses these issues by breaking instruction into **shorter steps**
 - o shorter instructions take fewer steps
 - o can re-use hardware
 - o cycle time is faster

Single- vs. Multicycle Processor

- **Single-cycle:**

- + simple
- cycle time limited by longest instruction (lw)
- separate memories for instruction and data
- 3 adders/ALUs

- **Multicycle:**


- + higher clock speed
- + simpler instructions run faster
- + reuse expensive hardware on multiple cycles
- sequencing overhead paid many times

**Same design steps
as single-cycle:**

- **first datapath**
- **then control**


Multicycle State Elements

 Replace separate Instruction and Data memories with a **single unified memory** – more realistic




Multicycle Datapath: Instruction Fetch

STEP 1: Fetch instruction

 


Multicycle Datapath: lw Get Sources

 STEP 2: Read source operand from RF and extend immediate




Multicycle Datapath: Lw Address

STEP 3: Compute the memory address

 


Multicycle Datapath: L_w Memory Read

STEP 4: Read data from memory

 


Multicycle Datapath: 1_W Write Register

STEP 5: Write data back to register file

 

Multicycle Datapath: Increment PC

STEP 6: Increment PC: $PC = PC + 4$

 


Chapter 7: Microarchitecture

Multicycle Datapath: Other Instructions


Multicycle Datapath: SW

Write data in **rs2** to memory

 


Multicycle Datapath: beq

 Calculate branch target address:
 $BTA = PC + imm$



PC is updated in Fetch stage, so need to save **old (current) PC**

Multicycle RISC-V Processor

 


Chapter 7: Microarchitecture


Multicycle Control

Multicycle Control


High-Level View

 

Low-Level View

 


Multicycle Control: Instruction Decoder

 

op	Instruction	ImmSrc
3	lw	00
35	sw	01
51	R-type	XX
99	beq	10


Multicycle Control: Main FSM

 


To declutter FSM:

- **Write enable signals** (RegWrite, MemWrite, IRWrite, PCUpdate, and Branch) are **0** if not listed in a state.
- **Other signals are don't care** if not listed in a state


Main FSM: Fetch

 


Main FSM: Decode

 

Main FSM: Address

 


Main FSM: Read Memory

 


Main FSM: Read Memory Datapath

S3: MemRead
ResultSrc = 00
AdrSrc = 1


S3: MemRead

 

Main FSM: Write RF

 


Main FSM: Write RF Datapath

 


Main FSM: Fetch Revisited

 Calculate **PC+4**
during Fetch stage
(ALU isn't being
used)




Main FSM: Fetch (PC+4) Datapath

 


Chapter 7: Microarchitecture

Multicycle Control: Other Instructions


Main FSM: SW

 


Main FSM: sw Datapath

 


Main FSM: R-Type Execute

 


Main FSM: R-Type Execute Datapath

 

Main FSM: R-Type ALU Write Back

 


Main FSM: R-Type ALU Write Back

 

Main FSM: `beq`

- **Need to calculate:**
 - Branch Target Address
 - **rs1 - rs2** (to see if equal)
- **ALU** isn't being used in Decode stage
 - Use it to calculate Target Address ($PC + imm$)

Main FSM: Decode Revisited

 


Main FSM: Decode (Target Address)




S1: Decode
 ALUSrcA = 01
 ALUSrcB = 01
 ALUOp = 00

 Read Registers and Calculate Target Address (PC+imm)




Main FSM: beq

 

Main FSM: beq Datapath


**Compare registers and
Send Target PC (ALUOut) to PCNext**

 

Chapter 7: Microarchitecture

Extending the RISC-V Multicycle Processor

Main FSM: I-Type ALU Execute

 


Main FSM: I-Type ALU Exec. Datapath


S8: Executel

ALUSrcA = 10
ALUSrcB = 01
ALUOp = 10

S8: Executel

 


Main FSM: jal

 


Main FSM: jal Datapath

 Calculate PC + 4 and
Send Target Address (ALUOut) to PCNext




Main FSM: jal

 PC + 4 is
written to **rd**
in **S7: ALUWB**



Multicycle Processor Main FSM

State	Datapath	μ Op
Fetch	Instr Mem[PC]; PC	PC+4
Decode	ALUOut	PCtarget
MemAdr	ALUOut	rs1 + imm
MemRead	Data Mem[ALUOut]	
MemWB	rd	Data
MemWrite	Mem[ALUOut]	rd
ExecuteR	ALUOut	rs1 op rs2
ExecuteI	ALUOut	rs1 op imm
ALUWB	rd	ALUOut
BEQ	ALUResult = rs1-rs2; if Zero, PC	ALUOut
JAL	PC	ALUOut; ALUOut PC+4

 

Chapter 7: Microarchitecture

Multicycle Performance

Multicycle Processor Performance


- Instructions take different number of cycles:
 - 3 cycles: beq
 - 4 cycles: R-type, addi, sw, jal
 - 5 cycles: lw
- CPI is weighted average
- SPECINT2000 benchmark:
 - 25% loads
 - 10% stores
 - 13% branches
 - 52% R-type

$$\text{Average CPI} = (0.13)(3) + (0.52 + 0.10)(4) + (0.25)(5) = 4.12$$

Multicycle Critical Path

Potential Critical Paths:

- Calculate PC + 4 or
- Read Memory

 

Multicycle Processor Performance

Multicycle critical path:

- **Assumptions:**
 - RF is faster than memory
 - Writing memory is faster than reading memory

$$T_{c_multi} = t_{pcq} + t_{dec} + 2t_{mux} + \max(t_{ALU}, t_{mem}) + t_{setup}$$

Multicycle Performance Example

Element	Parameter	Delay (ps)
Register clock-to-Q	t_{pcq_PC}	40
Register setup	t_{setup}	50
Multiplexer	t_{mux}	30
AND-OR gate	t_{AND-OR}	20
ALU	t_{ALU}	120
Decoder (Control Unit)	t_{dec}	25
Extend unit	t_{dec}	35
Memory read	t_{mem}	200
Register file read	t_{RFread}	100
Register file setup	$t_{RFsetup}$	60

$$T_{c_multi} = t_{pcq} + t_{dec} + 2t_{mux} + \max(t_{ALU}, t_{mem}) + t_{setup}$$

$$=$$

Multicycle Performance Example

For a program with **100 billion** instructions executing on a **multicycle** RISC-V processor

- **CPI** = 4.12 cycles/instruction
- **Clock cycle time:** $T_{c_multi} = 375 \text{ ps}$

$$\text{Execution Time} = (\# \text{ instructions}) \times \text{CPI} \times T_c$$

This is **slower** than the single-cycle processor (75 sec.)

Chapter 7: Microarchitecture


Pipelined RISC-V Processor

Pipelined RISC-V Processor


- **Temporal parallelism**
- Divide single-cycle processor into **5 stages**:
 - Fetch
 - Decode
 - Execute
 - Memory
 - Writeback
- Add **pipeline registers** between stages

Single-Cycle vs. Pipelined Processor


Single-Cycle

 



Pipelined

 

Pipelined Processor Abstraction

 


Single-Cycle & Pipelined Datapaths

  


Signals in Pipelined Processor are appended with first letter of stage (i.e., PC_F, PC_D, PC_E).

Corrected Pipelined Datapath

 

- **Rd** must arrive at same time as **Result**
- Register file written on **falling edge** of CLK

Pipelined Processor with Control

 

- Same control unit as single-cycle processor
- Control signals travel with the instruction (drop off when used)


Chapter 7: Microarchitecture

Pipelined Processor Hazards

Pipelined Hazards

- When an instruction depends on result from instruction that hasn't completed
- Types:
 - **Data hazard:** register value not yet written back to register file
 - **Control hazard:** next instruction not decided yet (caused by branch)

Data Hazard

 


Handling Data Hazards

Stall the processor at run time


Handling Data Hazards

 - **Insert** enough **nops** for result to be ready
- Or move independent useful instructions forward




Data Forwarding

 - Data is **available on internal busses** before it is written back to the register file (RF).
- **Forward data** from internal busses **to Execute stage**.




Data Forwarding

 - Check if source register **in Execute stage matches** destination register of instruction **in Memory or Writeback stage**.
- If so, forward result.



Data Forwarding: Hazard Unit

 

Data Forwarding

- **Case 1: Execute** stage $Rs1$ or $Rs2$ matches **Memory** stage Rd ?
Forward from Memory stage
- **Case 2: Execute** stage $Rs1$ or $Rs2$ matches **Writeback** stage Rd ?
Forward from Writeback stage
- **Case 3:** Otherwise use value read from register file (as usual)

Equations for $Rs1$:

```
if      (( $Rs1E == RdM$ ) AND  $RegWriteM$ )           // Case 1
        ForwardAE = 10
else if (( $Rs1E == RdW$ ) AND  $RegWriteW$ )           // Case 2
        ForwardAE = 01
else    ForwardAE = 00                           // Case 3
```

ForwardBE equations are similar (replace $Rs1E$ with $Rs2E$)

Data Forwarding

- **Case 1: Execute** stage $Rs1$ or $Rs2$ matches **Memory** stage Rd ?
Forward from Memory stage
- **Case 2: Execute** stage $Rs1$ or $Rs2$ matches **Writeback** stage Rd ?
Forward from Writeback stage
- **Case 3:** Otherwise use value read from register file (as usual)

Equations for $Rs1$:


if $((Rs1E == RdM) \text{ AND } RegWriteM) \text{ AND } (Rs1E \neq 0) // \text{Case 1}$
ForwardAE = 10

else if $((Rs1E == RdW) \text{ AND } RegWriteW) \text{ AND } (Rs1E \neq 0) // \text{Case 2}$
ForwardAE = 01


else ForwardAE = 00 // Case 3

ForwardBE equations are similar (replace $Rs1E$ with $Rs2E$)

Data Hazard due to lw Dependency

 

Stalling to solve 1w Data Dependency

 

Stalling Logic

- Is either **source register in the Decode stage** the same as the **destination register in the Execute stage**?

AND


- Is the instruction in the **Execute stage** a **lw**?

$lwStall = ((Rs1D == RdE) \text{ OR } (Rs2D == RdE)) \text{ AND } ResultSrcE$ 0

$StallF = StallD = FlushE = lwStall$

(Stall the Fetch and Decode stages, and flush the Execute stage.)

Stalling Hardware

 


Chapter 7: Microarchitecture

Pipelined Processor Control Hazards

Control Hazards

- **beq:**
 - Branch **not determined** until the **Execute stage** of pipeline
 - **Instructions** after branch **fetched** before branch occurs
 - These **2 instructions must be flushed** if branch happens

Control Hazards

 

Branch misprediction penalty:

The number of instructions flushed when a branch is taken (in this case, 2 instructions)


Control Hazards: Flushing Logic

- If branch is taken in execute stage, need to flush the instructions in the Fetch and Decode stages
 - Do this by clearing Decode and Execute Pipeline registers using *FlushD* and *FlushE*
- **Equations:**


$$FlushD = PCSrcE$$

$$FlushE = lwStall \text{ OR } PCSrcE$$

Control Hazards: Flushing Hardware

 

 RISC-V Pipelined Processor with Hazard Unit



Summary of Hazard Logic

Data hazard logic (shown for SrcA of ALU):

```
if      ((Rs1E == RdM) AND RegWriteM) AND (Rs1E != 0)    // Case 1
        ForwardAE = 10
else if ((Rs1E == RdW) AND RegWriteW) AND (Rs1E != 0)    // Case 2
        ForwardAE = 01
else      ForwardAE = 00                                // Case 3
```

Load word stall logic:

```
lwStall = ((Rs1D == RdE) OR (Rs2D == RdE)) AND ResultSrcE    0
StallF = StallD = lwStall
```

Control hazard flush:

```
FlushD = PCSrcE
FlushE = lwStall OR PCSrcE
```

Chapter 7: Microarchitecture

Pipelined Performance

Pipelined Processor Performance Example

- **SPECINT2000 benchmark:**
 - 25% loads
 - 10% stores
 - 13% branches
 - 52% R-type
- **Suppose:**
 - 40% of loads used by next instruction
 - 50% of branches mispredicted
- **What is the average CPI?** (Ideally it's 1, but...)

= 1.23

Pipelined Processor Performance Example

Pipelined processor critical path:

$T_{c_pipelined} = \max \text{ of}$

$t_{pcq} + t_{mem} + t_{setup}$

$2(t_{Rfread} + t_{setup})$

$t_{pcq} + 4t_{mux} + t_{ALU} + t_{AND-OR} + t_{setup}$


$t_{pcq} + t_{mem} + t_{setup}$

$2(t_{pcq} + t_{mux} + t_{RFwrite})$

Fetch
Decode
Execute
Memory
Writeback

- Decode and Writeback stages **both use the register file** in each cycle
- So each stage gets half of the cycle time ($T_c/2$) to do their work
- Or, stated a different way, **2x of their work** must fit in a cycle (T_c)

Pipelined Critical Path: Execute Stage

 

Pipelined Performance Example

Element	Parameter	Delay (ps)
Register clock-to-Q	t_{pcq_PC}	40
Register setup	t_{setup}	50
Multiplexer	t_{mux}	30
AND-OR gate	t_{AND-OR}	20
ALU	t_{ALU}	120
Decoder (Control Unit)	t_{dec}	25
Extend unit	t_{dec}	35
Memory read	t_{mem}	200
Register file read	t_{RFread}	100
Register file setup	$t_{RFsetup}$	60

$$T_{c_pipelined} = t_{pcq} + 4t_{mux} + t_{ALU} + t_{AND-OR} + t_{setup}$$

$$=$$

Pipelined Performance Example

Program with 100 billion instructions

$$\begin{aligned}\text{Execution Time} &= (\# \text{ instructions}) \times \text{CPI} \times T_c \\ &= (100 \times 10^9)(1.23)(350 \times 10^{-12}) \\ &= \mathbf{43 \text{ seconds}}\end{aligned}$$

Processor Performance Comparison

Processor	Execution Time (seconds)	Speedup (single-cycle as baseline)
Single-cycle	75	1
Multicycle	155	0.5
Pipelined	43	1.7

Chapter 7: Microarchitecture


Advanced Microarchitecture

Advanced Microarchitecture

- Deep Pipelining
- Micro-operations
- Branch Prediction
- Superscalar Processors
- Out of Order Processors
- Register Renaming
- SIMD
- Multithreading
- Multiprocessors

Deep Pipelining

 - **10-20 stages typical**
- Number of stages limited by:
 - Pipeline hazards
 - Sequencing overhead
 - Power
 - Cost



Micro-operations

- Decompose complex instructions into series of simple instructions called **micro-operations** (*micro-ops* or μ -ops)
- **At run-time**, complex instructions are decoded into one or more micro-ops
- Used heavily in **CISC** (complex instruction set computer) architectures (e.g., x86)

Complex Op

```
lw s1, 0(s2), postincr 4
```

Micro-op Sequence

```
lw    s1, 0(s2)
addi  s2, s2, 4
```

Without μ -ops, would need 2nd write port on the register file

Branch Prediction

- **Guess** whether branch will be taken
 - Backward branches are usually taken (loops)
 - Consider history to improve guess
- Good prediction **reduces fraction of branches requiring a flush**

Branch Prediction

- Ideal pipelined processor: $CPI = 1$
- Branch misprediction increases CPI
- **Static branch prediction:**
 - Check direction of branch (forward or backward)
 - If backward, predict taken
 - Else, predict not taken
- **Dynamic branch prediction:**
 - Keep **history** of last several hundred (or thousand) branches in *branch target buffer*, record:
 - Branch destination
 - Whether branch was taken

Dynamic Branch Prediction

- 1-bit branch predictor
- 2-bit branch predictor

Branch Prediction Example

```
addi s1, zero, 0      # s1 = sum
addi s0, zero, 0      # s0 = i
addi t0, zero, 10     # t0 = 10
```

```
For:                  # for (i=0; i<10; i=i+1)
    bge    s0, t0, Done
    add    s1, s1, s0    # sum = sum + i
    addi   s0, s0, 1     # i = i + 1
    j      For
```

Done:

1-Bit Branch Predictor


- **Remembers** whether branch was taken the last time and **does the same thing**
- Mispredicts first and last branch of loop

```
addi s1, zero, 0      # s1 = sum
addi s0, zero, 0      # s0 = i
addi t0, zero, 10     # t0 = 10
```

```
For:                  # for (i=0; i<10; i=i+1)
    bge    s0, t0, Done
    add    s1, s1, s0    # sum = sum + i
    addi   s0, s0, 1     # i = i + 1
    j      For
```

Done:

2-Bit Branch Predictor

 

```
addi s1, zero, 0      # s1 = sum
addi s0, zero, 0      # s0 = i
addi t0, zero, 10     # t0 = 10
```

```
For:                  # for (i=0; i<10; i=i+1)
    bge    s0, t0, Done
    add    s1, s1, s0   # sum = sum + i
    addi   s0, s0, 1    # i = i + 1
j         For
```

Done:


Only mispredicts **last branch** of loop

Chapter 7: Microarchitecture

Superscalar & Out of Order Processors

Superscalar Processors

 - Multiple copies of datapath execute multiple instructions at once
- Dependencies make it tricky to issue multiple instructions at once



Superscalar Example

Ideal IPC: 2

Actual IPC: 2

lw s7, 40(s0)


add s8, t1, t2

sub s9, s1, s3

and s10, s3, t4

or s11, s1, t5

sw s5, 80(s2)

 

Superscalar with Dependencies

Ideal IPC:

2

Actual IPC:

$6/5 = 1.2$

lw s8, 40(s0)


add s9, s8, t1

sub s8, t2, t3

and s10, s4, s8

or s11, t5, t6

sw s7, 80(s11)

 

Out of Order (OOO) Processor

- Looks ahead across multiple instructions
- Issues as many instructions as possible at once
- Issues instructions out of order (as long as no dependencies)
- **Dependencies:**
 - **RAW** (read after write): one instruction writes, later instruction reads a register
 - **WAR** (write after read): one instruction reads, later instruction writes a register
 - **WAW** (write after write): one instruction writes, later instruction writes a register

Out of Order (OOO) Processor

- **Instruction level parallelism (ILP):** number of instruction that can be issued simultaneously (average < 3)
- **Scoreboard:** table that keeps track of:
 - Instructions waiting to issue
 - Available functional units
 - Dependencies

Out of Order Processor Example


Ideal IPC: 2

Actual IPC: $6/4 = 1.5$

lw s8, 40(s0)
or s11, t5, t6
sw s7, 80(s11)
add s9, s8, t1
sub s8, t2, t3
and s10, s4, s8

two cycle latency
between load and
use of s8

RAW
WAR
RAW

 


Register Renaming

Ideal IPC: 2


Actual IPC: $6/3 = 2$

 lw s8, 40(s0)
sub r0, t2, t3
2-cycle RAW and s10, s4, r0
or s11, t5, t6
add s9, s8, t1
sw s7, 80(s11)



SIMD

- **Single Instruction Multiple Data (SIMD)**
 - Single instruction **acts on multiple pieces of data at once**
 - Common application: **graphics**
 - Can apply to short arithmetic operations (also called *packed arithmetic*)
- For example, add eight 8-bit elements

 

Chapter 7: Microarchitecture

Multithreading & Multiprocessors

Advanced Architecture Techniques

- **Multithreading**
 - Wordprocessor: thread for typing, spell checking, printing
- **Multiprocessors**
 - Multiple processors (cores) on a single chip

Threading: Definitions

- **Process:** program running on a computer
 - Multiple processes can run at once: e.g., surfing Web, playing music, writing a paper
- **Thread:** part of a program
 - Each process has multiple threads: e.g., a word processor may have threads for typing, spell checking, printing

Threads in a Conventional Processor

Single-core system:

- One thread runs at once
- When one thread stalls (for example, waiting for memory):
 - Architectural state of that thread stored
 - Architectural state of waiting thread loaded into processor and it runs
 - Called **context switching**
- Appears to user like all threads running simultaneously

Multithreading

- Multiple copies of architectural state
- Multiple threads **active** at once:
 - When one thread stalls, another runs immediately
 - If one thread can't keep all execution units busy, another thread can use them
- Does not increase instruction-level parallelism (ILP) of single thread, but increases throughput

Intel calls this “hyperthreading”

Multiprocessors

- Multiple processors (cores) with a method of communication between them
- Types:
 - **Homogeneous:** multiple cores with shared main memory
 - **Heterogeneous:** separate cores for different tasks (for example, DSP and CPU in cell phone)
 - **Clusters:** each core has own memory system

About these Notes

Digital Design and Computer Architecture Lecture Notes

© 2021 Sarah Harris and David Harris

These notes may be used and modified for educational and/or non-commercial purposes so long as the source is attributed.